



# **Computer Hardware Engineering (IS1200)**

## **Computer Organization and Components (IS1500)**

Spring 2023


### **Lecture 9: ALU and Single-Cycle Processors**

Artur Podobas<sup>1</sup> (IS1500), Marco Chiesa<sup>2</sup> (IS1200)

<sup>1</sup>Assistant Professor, KTH Royal Institute of Technology

<sup>2</sup>Associate Professor, KTH Royal Institute of Technology

 
Slides by David Broman (extensions by Artur Podobas), KTH




# Course Structure



## Module 1: C and Assembly Programming

 

## Module 4: Processor Design

 

## Module 2: I/O Systems



## Module 5: Memory Hierarchy



## Module 3: Logic Design (IS1500 only)

**PROJ  
START**



## Module 6: Parallel Processors and Programs



**Proj. Expo**


**LE14**

**Part I**  
Arithmetic  
Logic Unit

**Part II**  
Data Path in a  
Single-Cycle Processor

**Part III**  
Control Unit in a  
Single-Cycle Processor

# Abstractions in Computer Systems

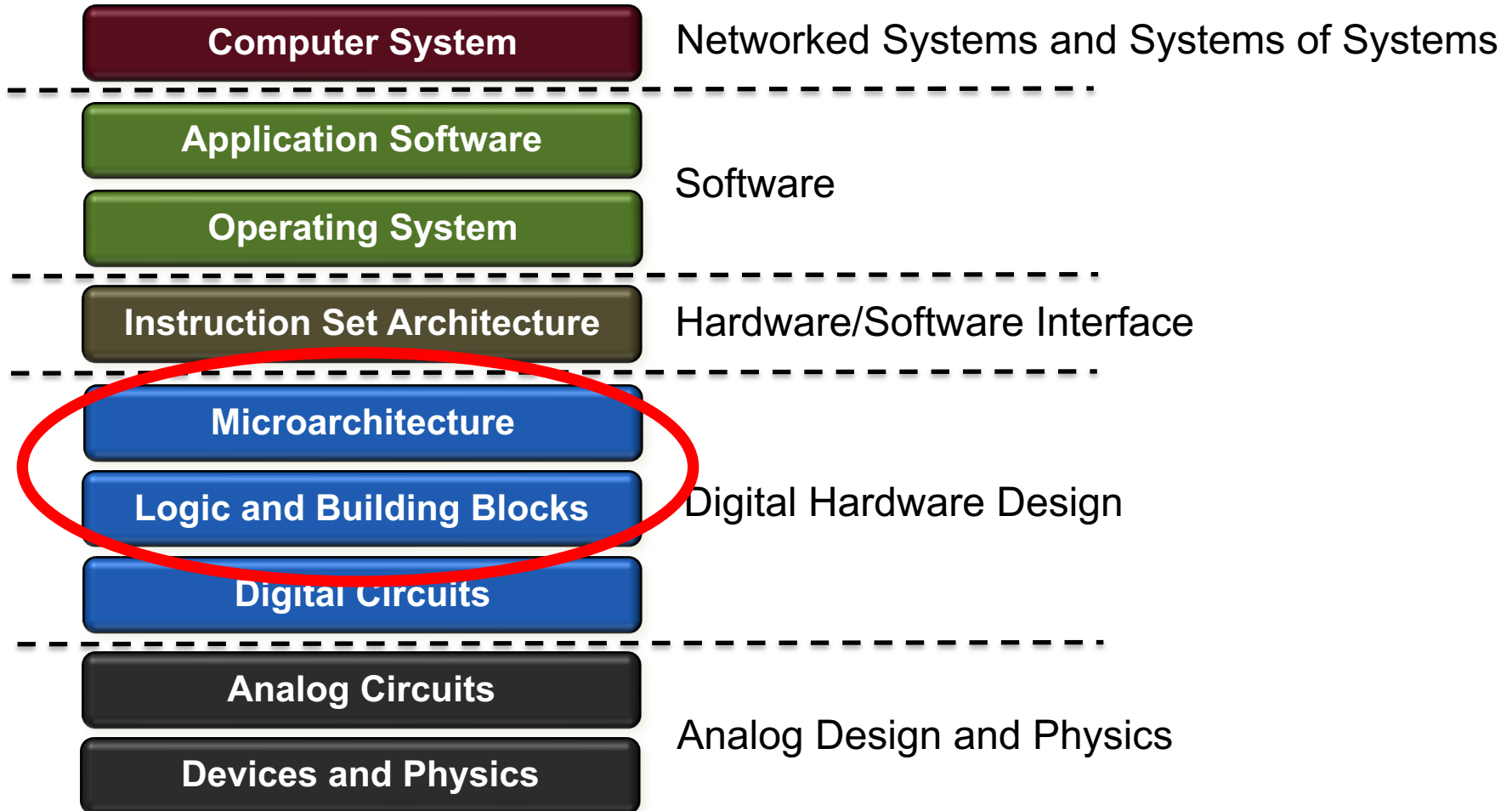

Part I  
Arithmetic  
Logic Unit

Part II  
Data Path in a  
Single-Cycle Processor

Part III  
Control Unit in a  
Single-Cycle Processor

# Agenda


## Part I

### Arithmetic Logic Unit



## Part II
 
### Data Path in a Single-Cycle Processor



## Part III

### Control Unit in a Single-Cycle Processor



Part I  
Arithmetic  
Logic Unit

Part II  
Data Path in a  
Single-Cycle Processor

Part III  
Control Unit in a  
Single-Cycle Processor

# Part I

## Arithmetic Logic Unit



Acknowledgement: The structure and several of the good examples are derived from the book “Digital Design and Computer Architecture” (2013) by D. M. Harris and S. L. Harris.





**Part I**  
Arithmetic  
Logic Unit

**Part II**  
Data Path in a  
Single-Cycle Processor

**Part III**  
Control Unit in a  
Single-Cycle Processor
  
# Arithmetic Logic Unit (ALU)

An **ALU** (sv. *Aritmetisk Logisk Enhet*) saves hardware by combining different arithmetic and logic operations in one single unit/element.



Input **F** specifies the function that the ALU should perform

ALUs can have different functions and be designed differently.

ALU symbol: both figures have the same function

An ALU can also include **output flags**, for instance:

- **Overflow flag** (adder overflowed)
- **Zero flag** (output is zero)
- **Negative flag** (if the value is negative)
- **Carry flag** (result of addition)



**Part I**  
Arithmetic  
Logic Unit


**Part II**  
Data Path in a  
Single-Cycle Processor

**Part III**  
Control Unit in a  
Single-Cycle Processor

# Arithmetic Logic Unit (ALU)
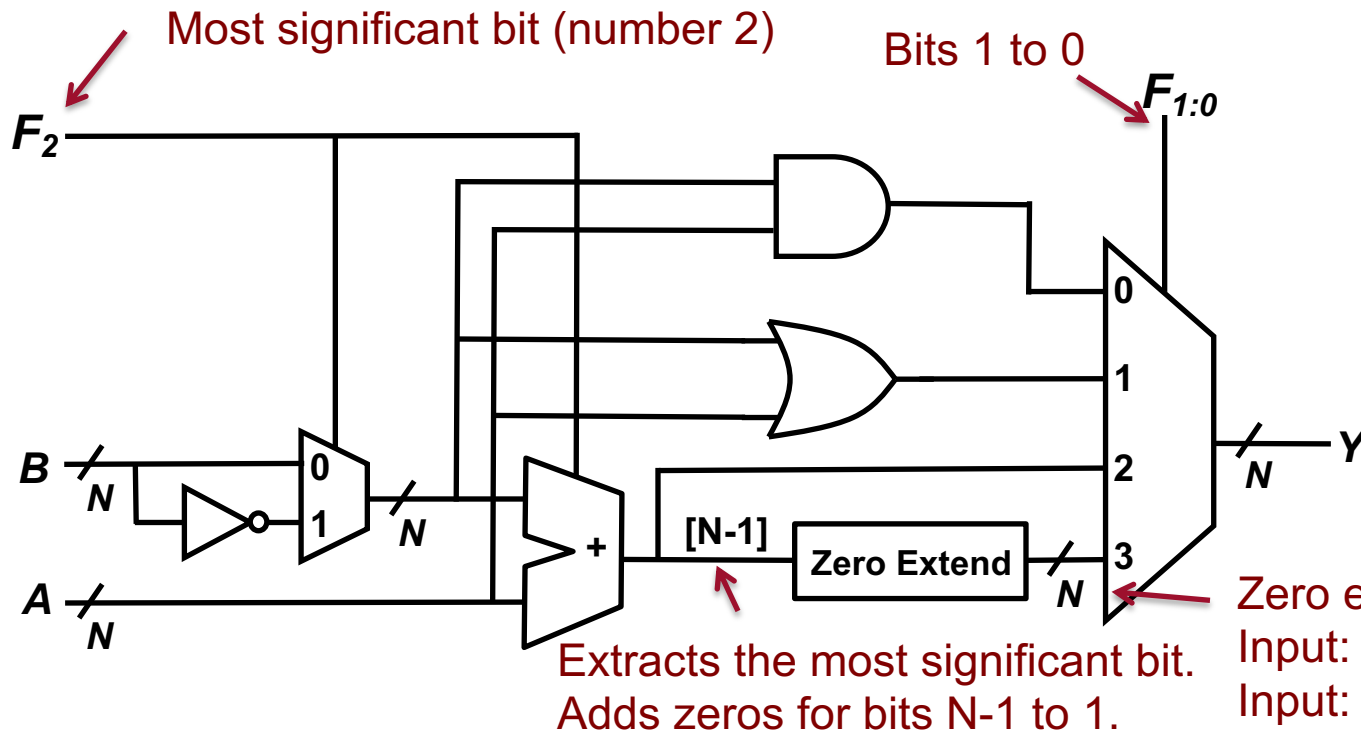
## Exercise:

Determine the functional behavior for each value of **F**.



$F_{2:0}$	Function
000	A AND B
001	A OR B
010	A + B
011	not used
100	A AND !B
101	A OR !B
110	A - B
111	SLT




Part I  
Arithmetic  
Logic Unit

Part II  
Data Path in a  
Single-Cycle Processor

Part III  
Control Unit in a  
Single-Cycle Processor

# Part II

## Data Path in a Single-Cycle Processor

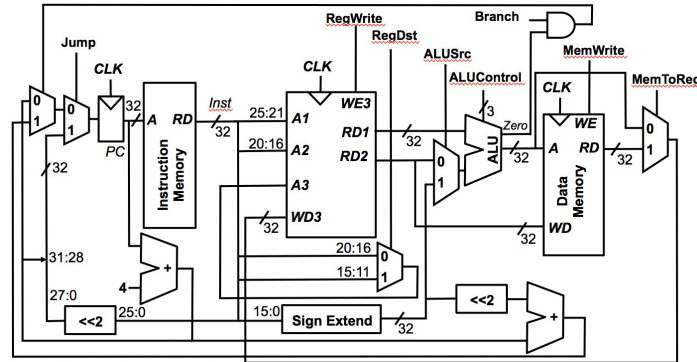


Acknowledgement: The structure and several of the good examples are derived from the book “Digital Design and Computer Architecture” (2013) by D. M. Harris and S. L. Harris.


 
# Data Path and Control Unit

A processor is typically divided into two parts



## Data Path

- Operates on a word of data.
- Consists of elements such as registers, memory, ALUs etc.



## Control Unit

- Gets the current instruction from the data path and tells the data path how to execute the instruction.

# Instructions

In this lecture, we construct a microarchitecture for a subset of a MIPS processor with the following instructions

**R-Type:** add, sub, and, or, slt

Arithmetic / logic instructions

Memory instructions

**I-Type:** addi, lw, sw, beq

Arithmetic  
immediate  
instruction

Branch instructions


**J-Type:** j



# State Elements (1/3)


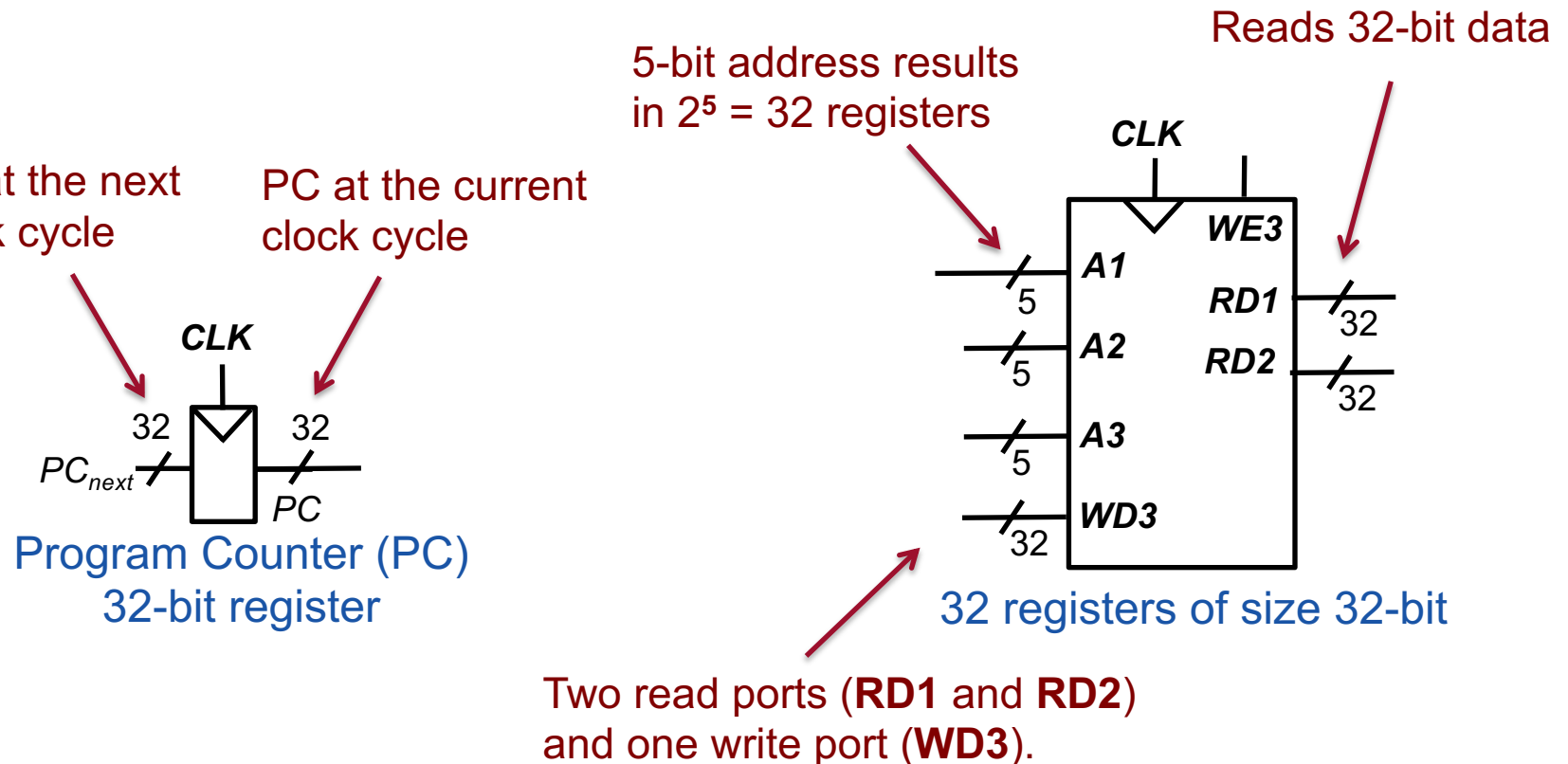
## Program Counter and Register File

The **architectural states** for this MIPS processor are the program counter (PC) and the 32 registers (\$0, \$t0, ... \$s0, \$s1, ... etc.)



# State Elements (2/3)

## Instructions and Data Memories

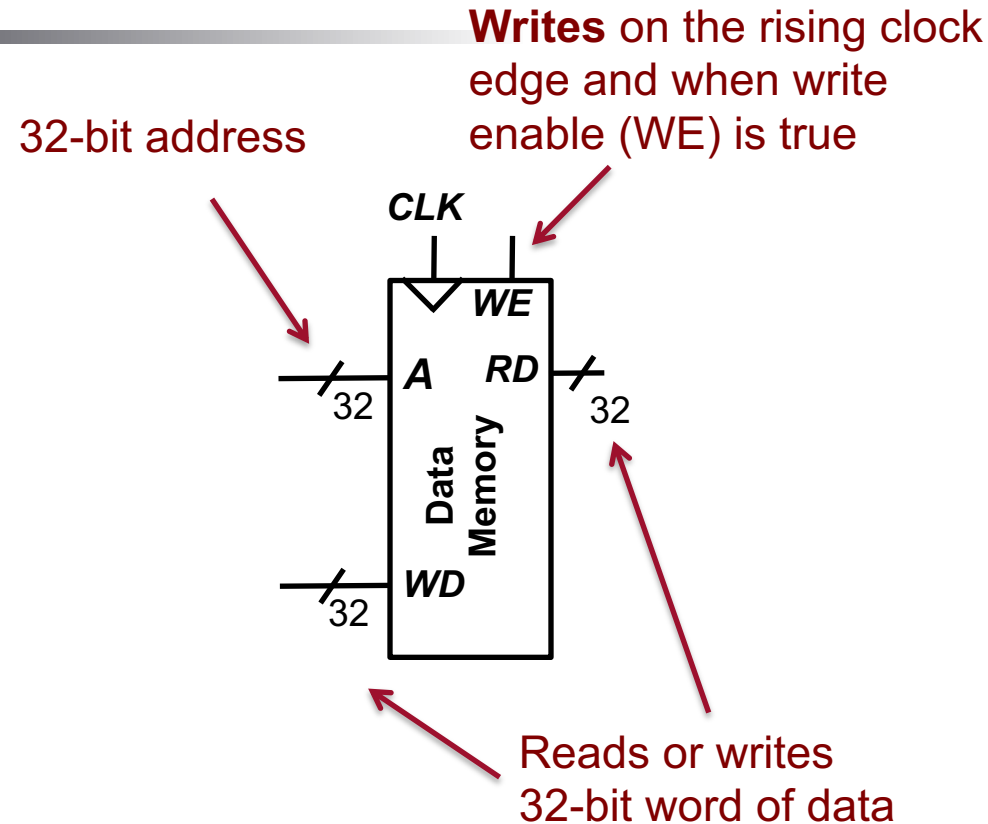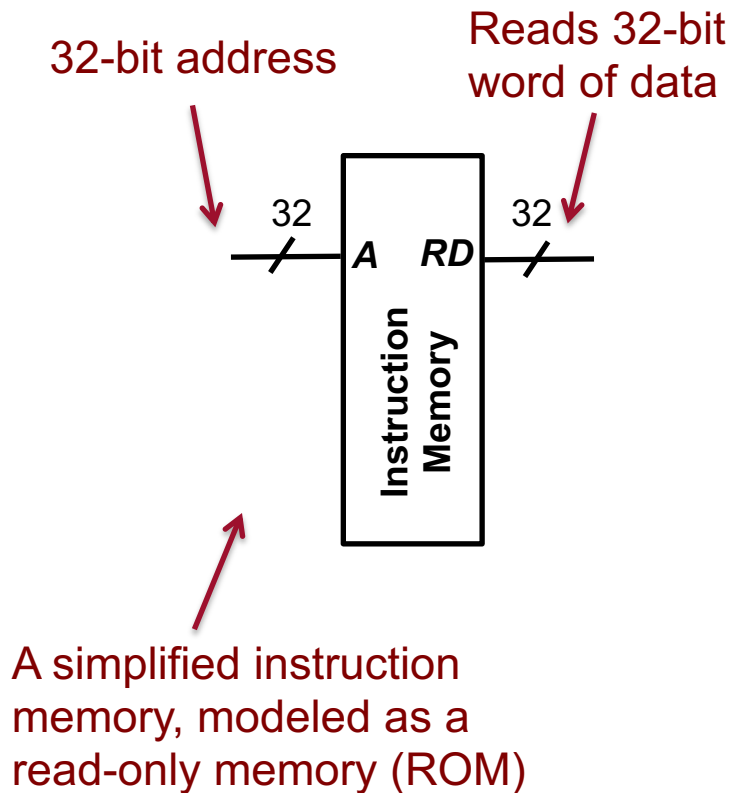

**Non-architectural states** are used to simplify logic or improve performance (introduced in the next lecture).


# State Elements (3/3)

## Reading combinationally, writing at clock edge


All the blocks below **read** *combinationally*: when the address changes, the data on the read port change after some propagation time.

There is no clock involved.

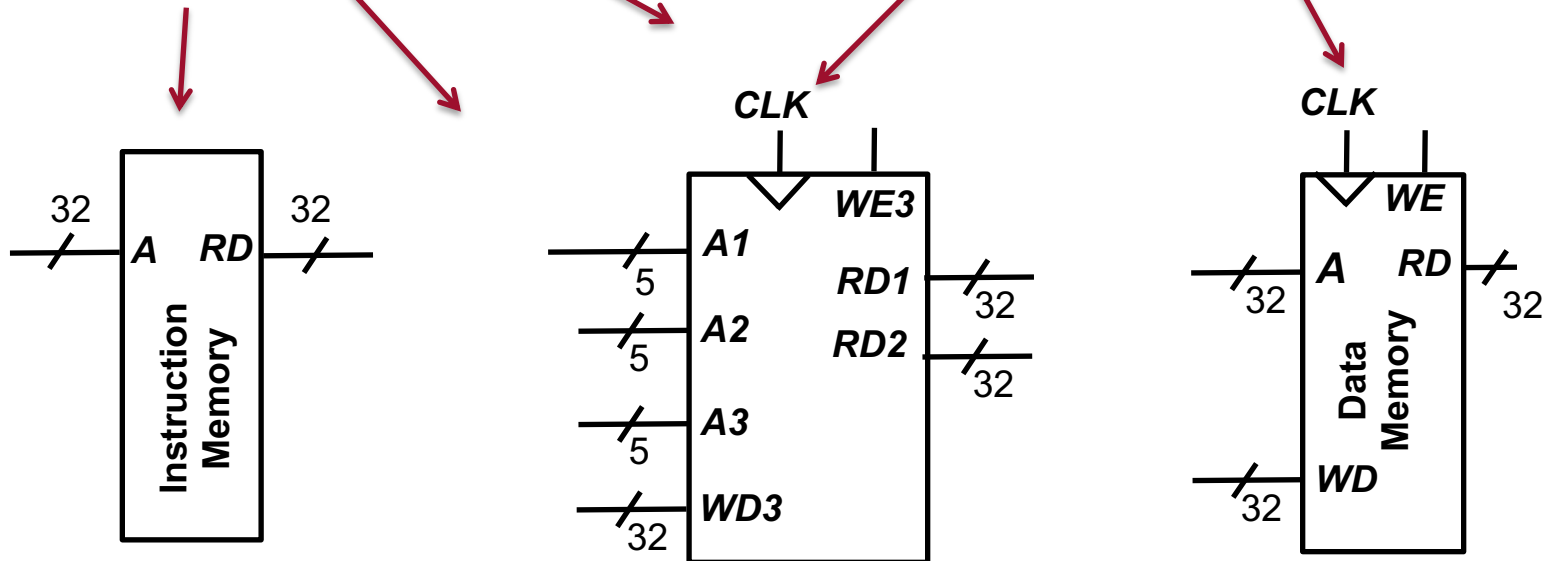The register file and the data memory **write** at the raising clock edge.




# Read Instruction from the Current PC

 

First step. Read the instruction at the current PC address.

A 32-bit instruction *Inst* is **fetched**.

# lw instruction – Read Base Address

 


Example

lw \$s0, 4(\$s1)

Read out the base address from the register file. 25:21 cuts out the 5 bits from the instruction.


Base address in **rs**

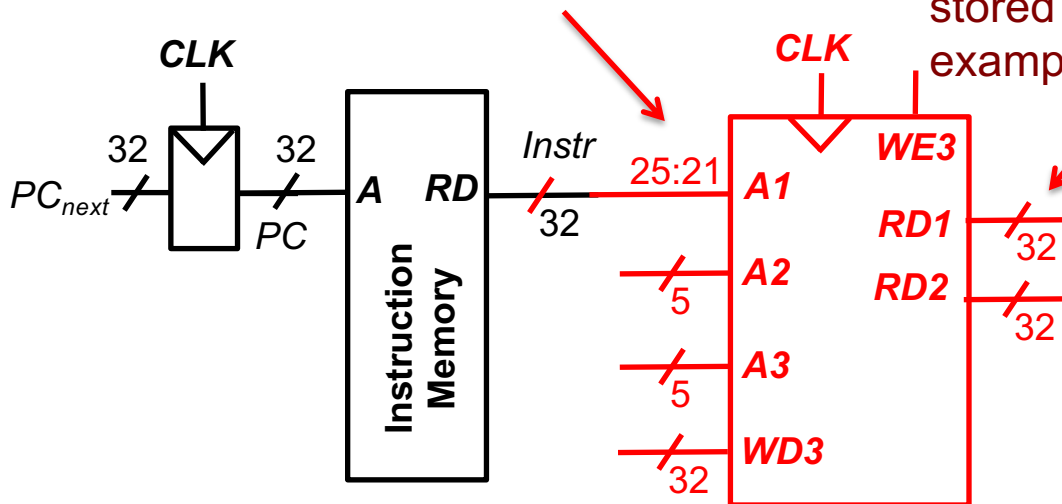RD1 holds the address stored in \$s1 (in the above example).



Loads the value from memory \$s1+4 and stores the result in \$s0.


# lw instruction – Read Offset

 

## Example

lw \$s0, 4(\$s1)

The offset is stored in the imm field.

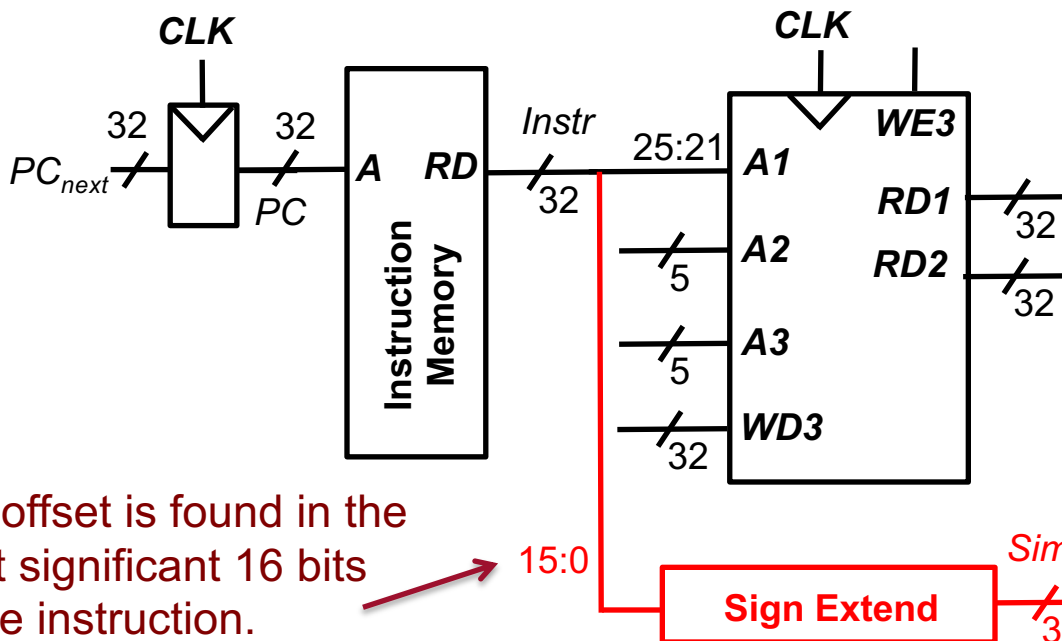


The offset is signed.  
Sign extend to 32 bits.


That is:  
 $Simm_{15:0} = Instr_{15:0}$   
 $Simm_{31:16} = Instr_{15}$



# lw instruction – Read Data Word

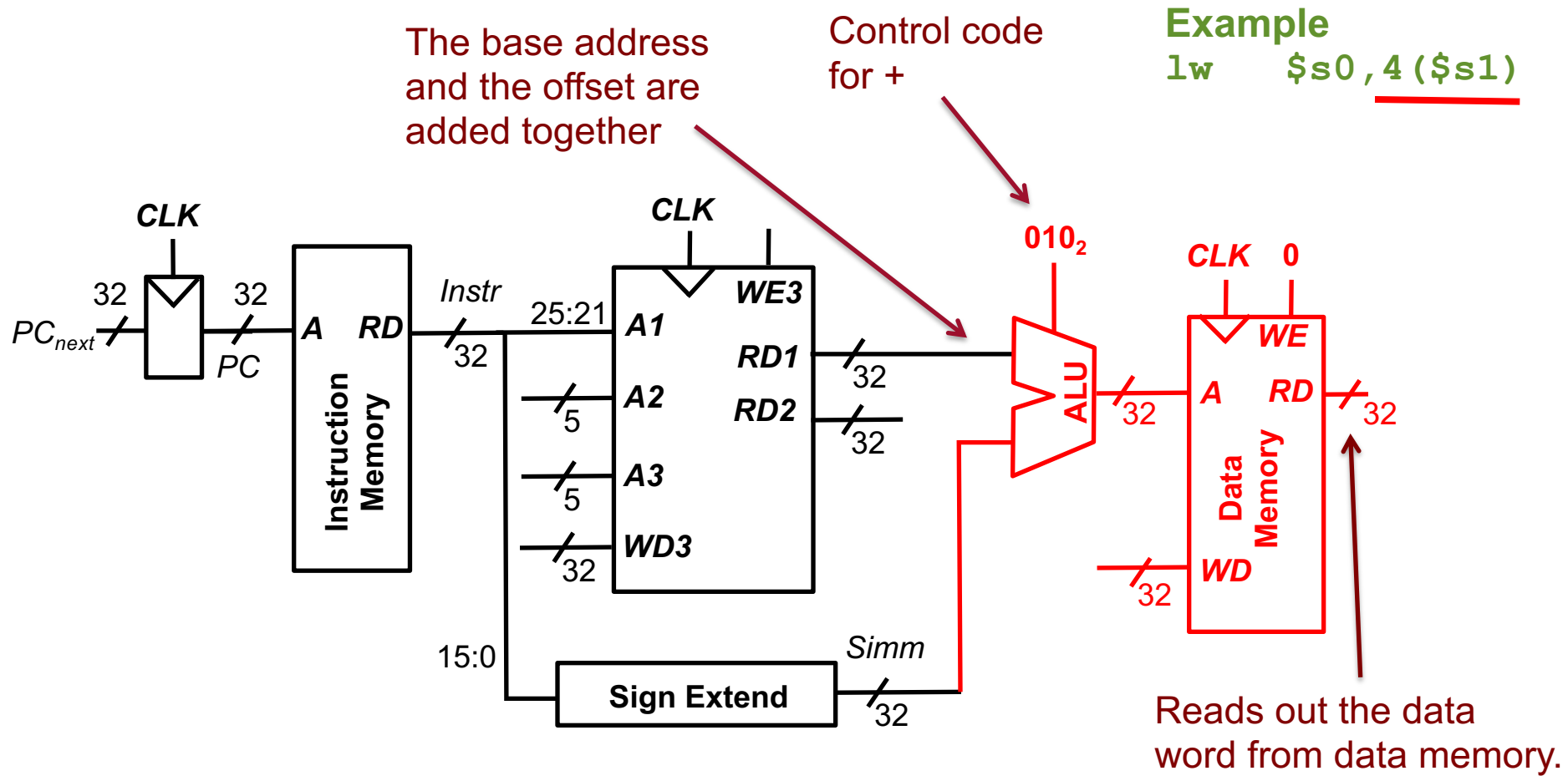


# lw instruction – Write Back

 


Example

lw \$s0, 4(\$s1)

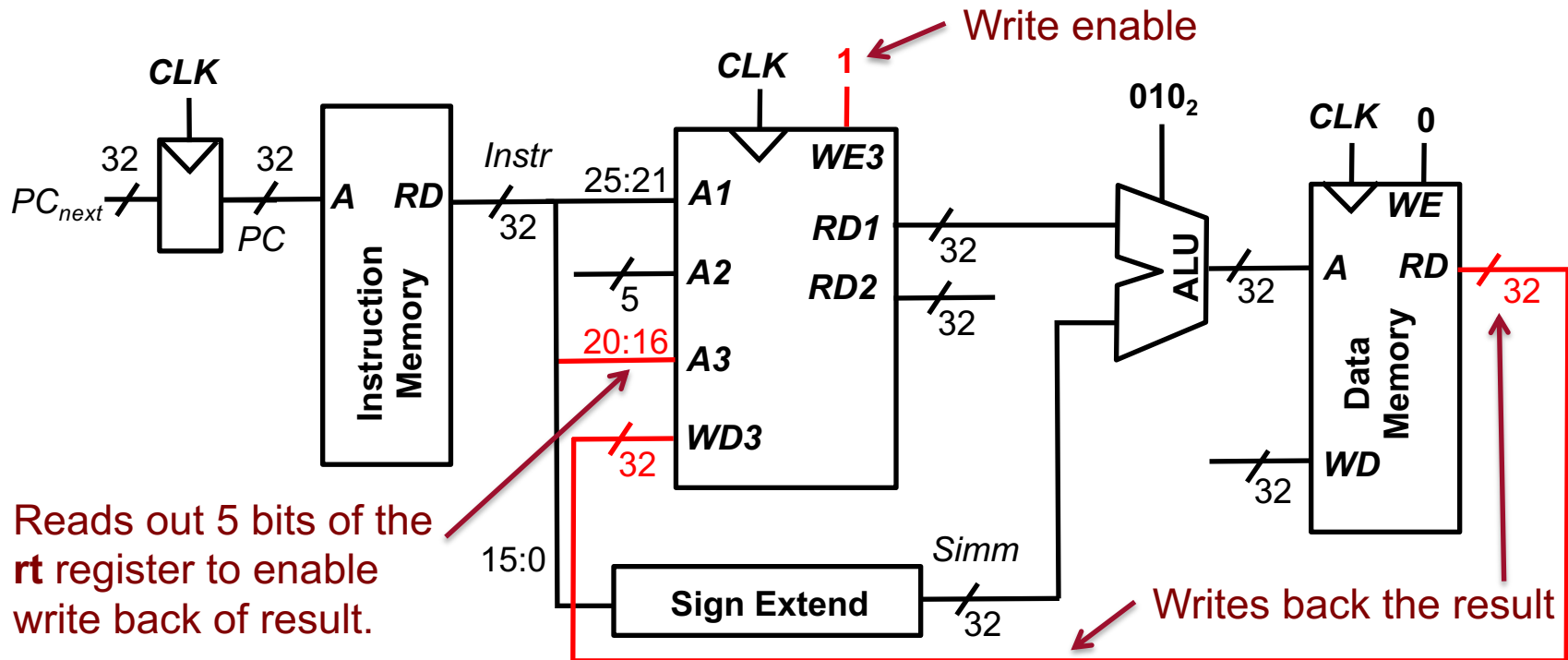


# 1w instruction – Increment PC

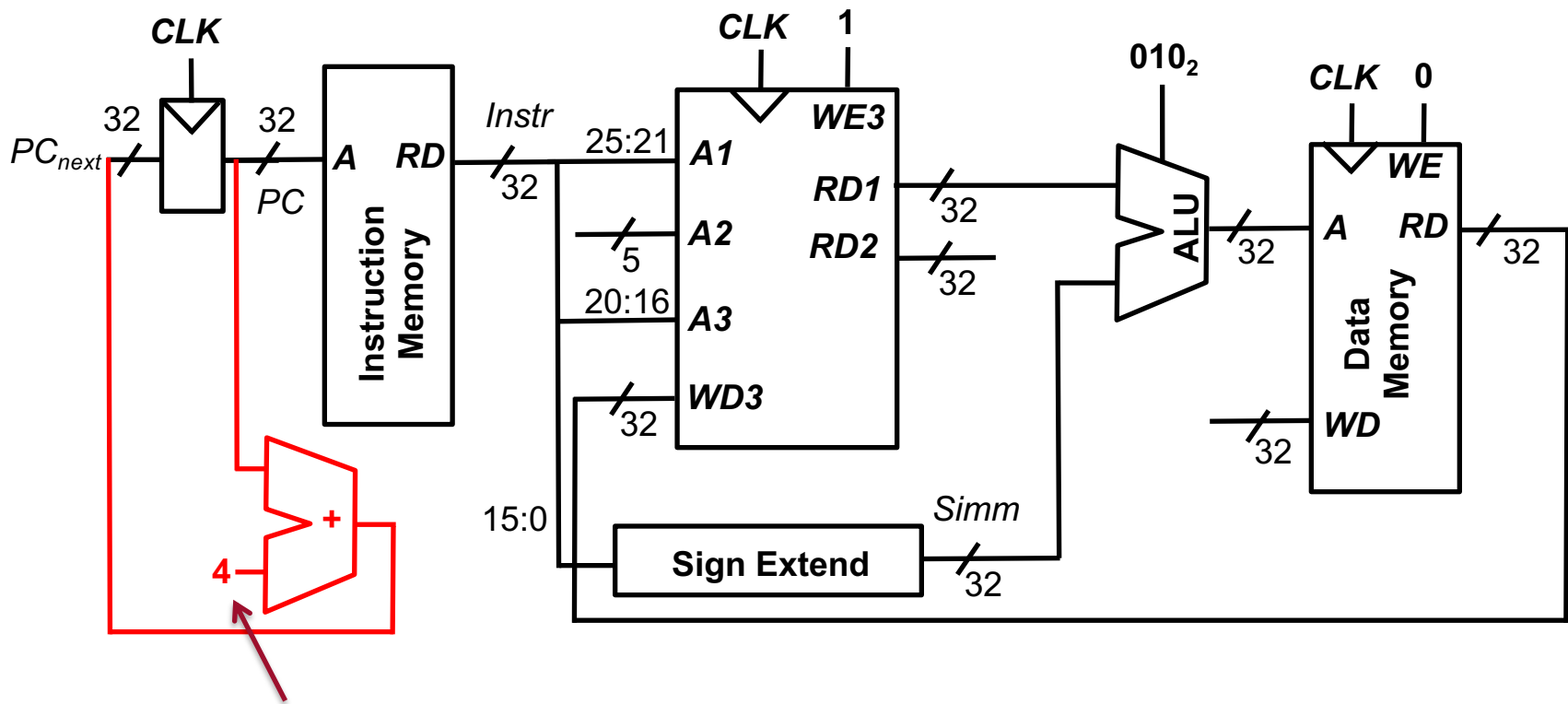

Increment the PC by 4.  
(Next instruction is at address PC + 4)

This is the complete data path for the load word (1w) instruction.


# 1w instruction – Timing

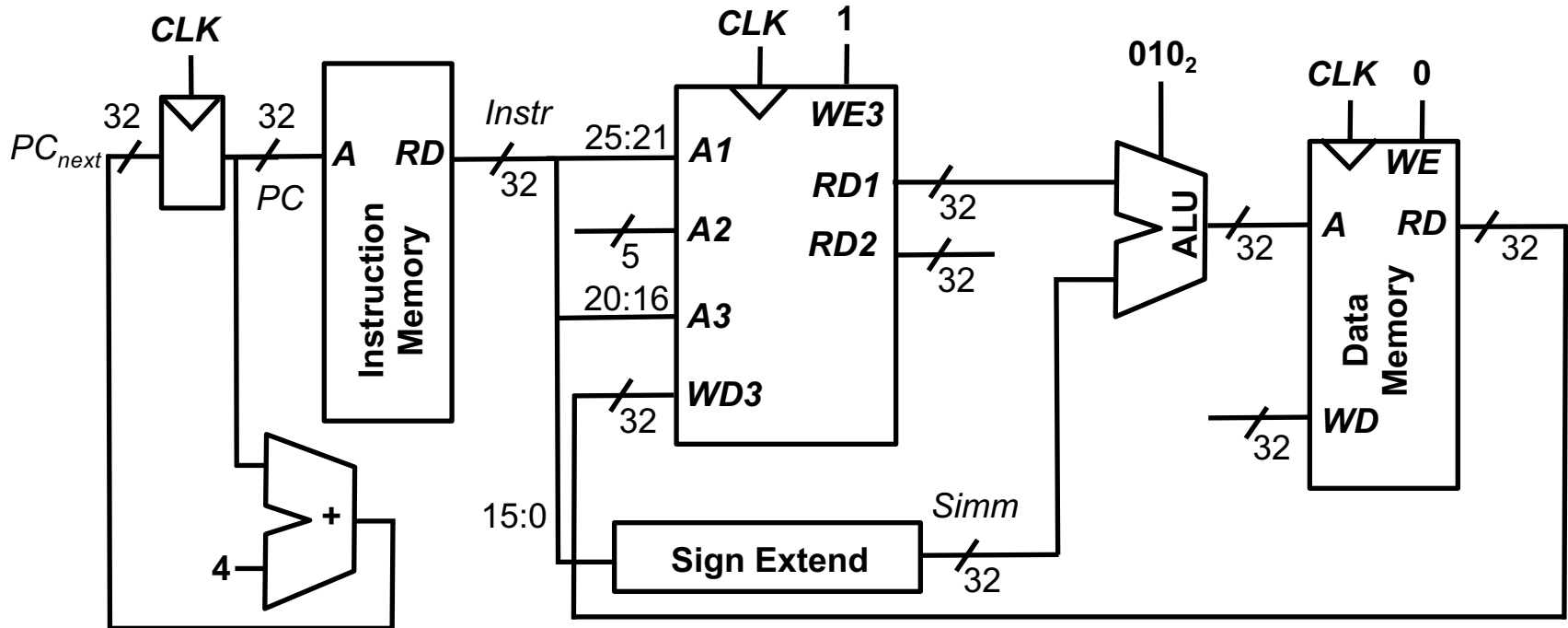

Combinational logic during clock cycle:  
read instruction, sign extend, read from  
register file, perform ALU operation, and  
read from the data memory.

At the raising clock edge:  
Write to the register file  
and update the PC.

CLK

 

Part I  
Arithmetic  
Logic Unit



Part II  
Data Path in a  
Single-Cycle Processor

Part III  
Control Unit in a  
Single-Cycle Processor

# sw instruction – Increment PC

We need to read the base address, read the offset, and compute an address. Good news: **We have already done that!**


## Example

sw \$s0, 4(\$s1)

The word to be stored is saved in a register (**rt**-field in the I-type)

Write enable must be false

The data word is stored into the memory

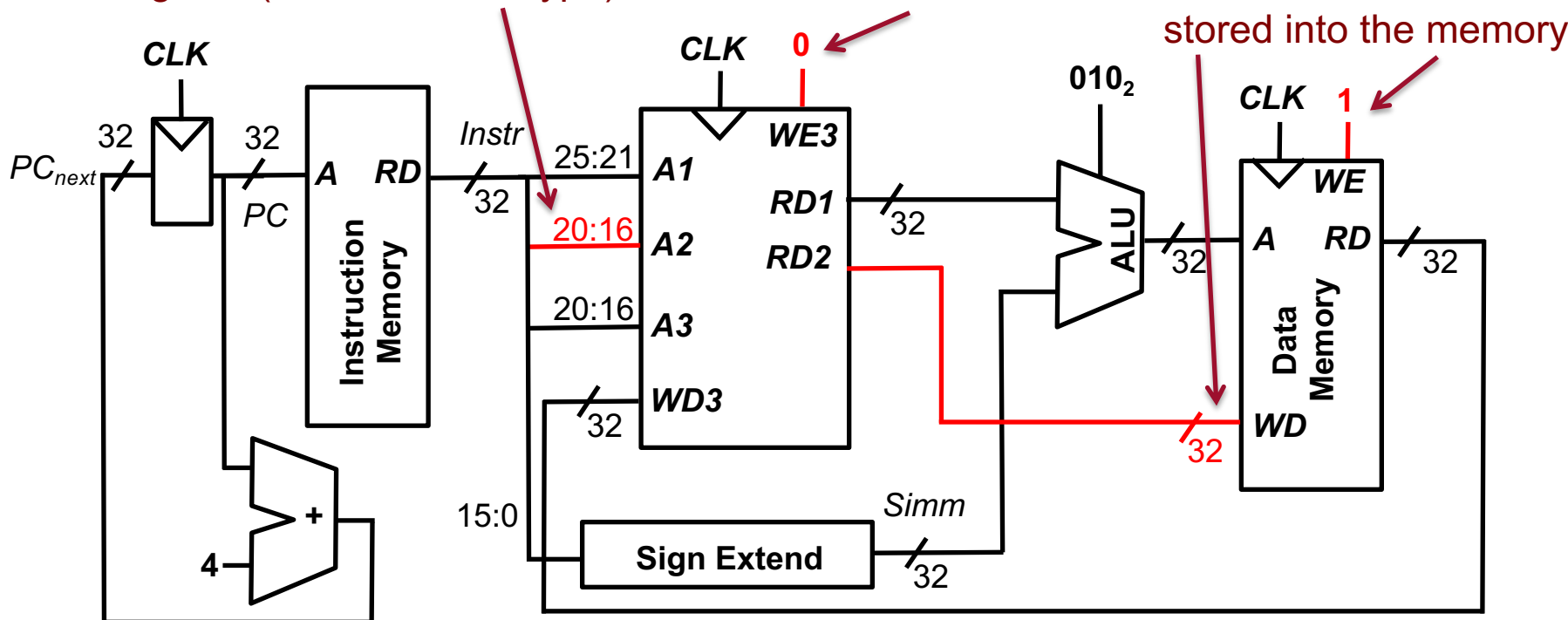

Part I  
Arithmetic  
Logic Unit




Part II  
Data Path in a  
Single-Cycle Processor

Part III  
Control Unit in a  
Single-Cycle Processor
 
# R-type instructions – Machine Encoding


We are now going to handle all R-type instructions the same uniform way.  
That is, we should handle **add**, **sub**, **and**, **or**, and **slt**.


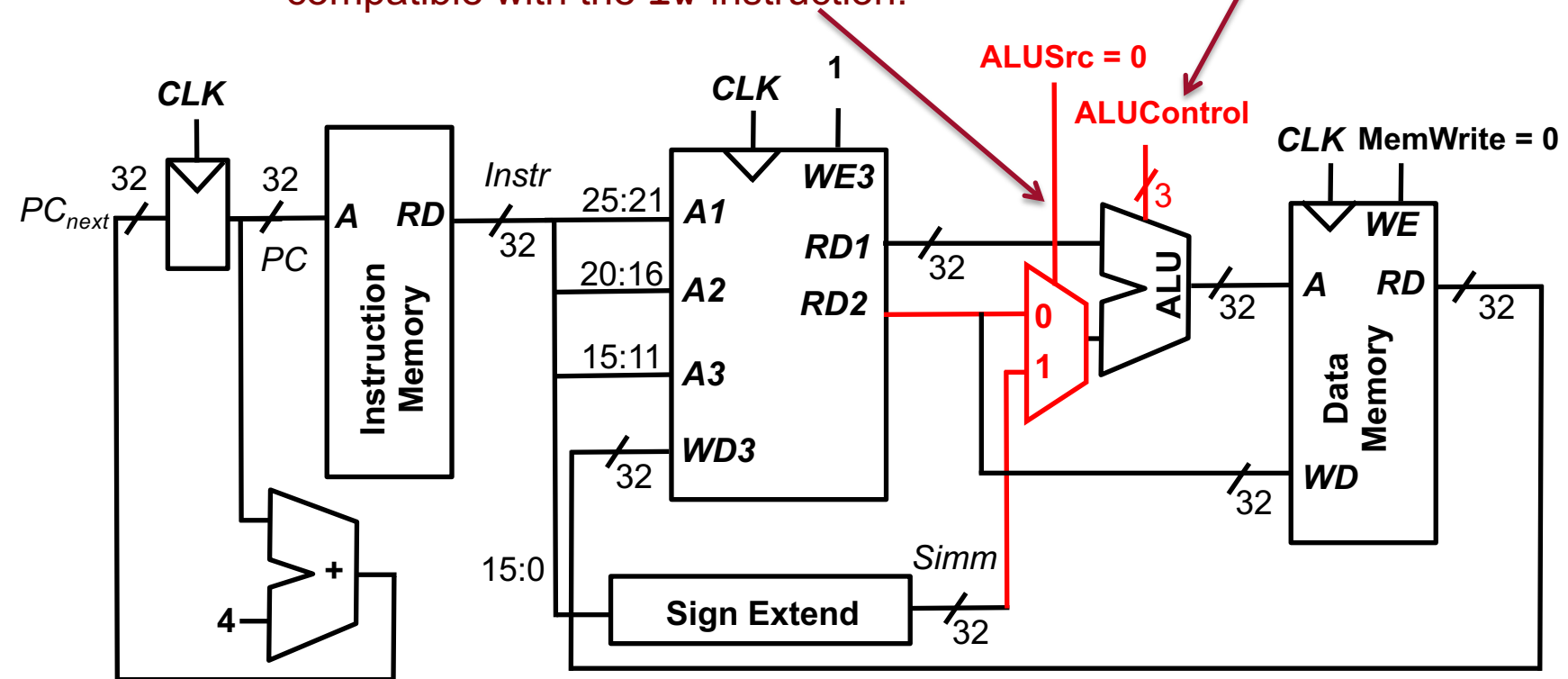
# R-type instructions – ALU Usage

We want to send the second operand to the ALU, but still be compatible with the lw-instruction.


Different ALU control signals for different instructions.


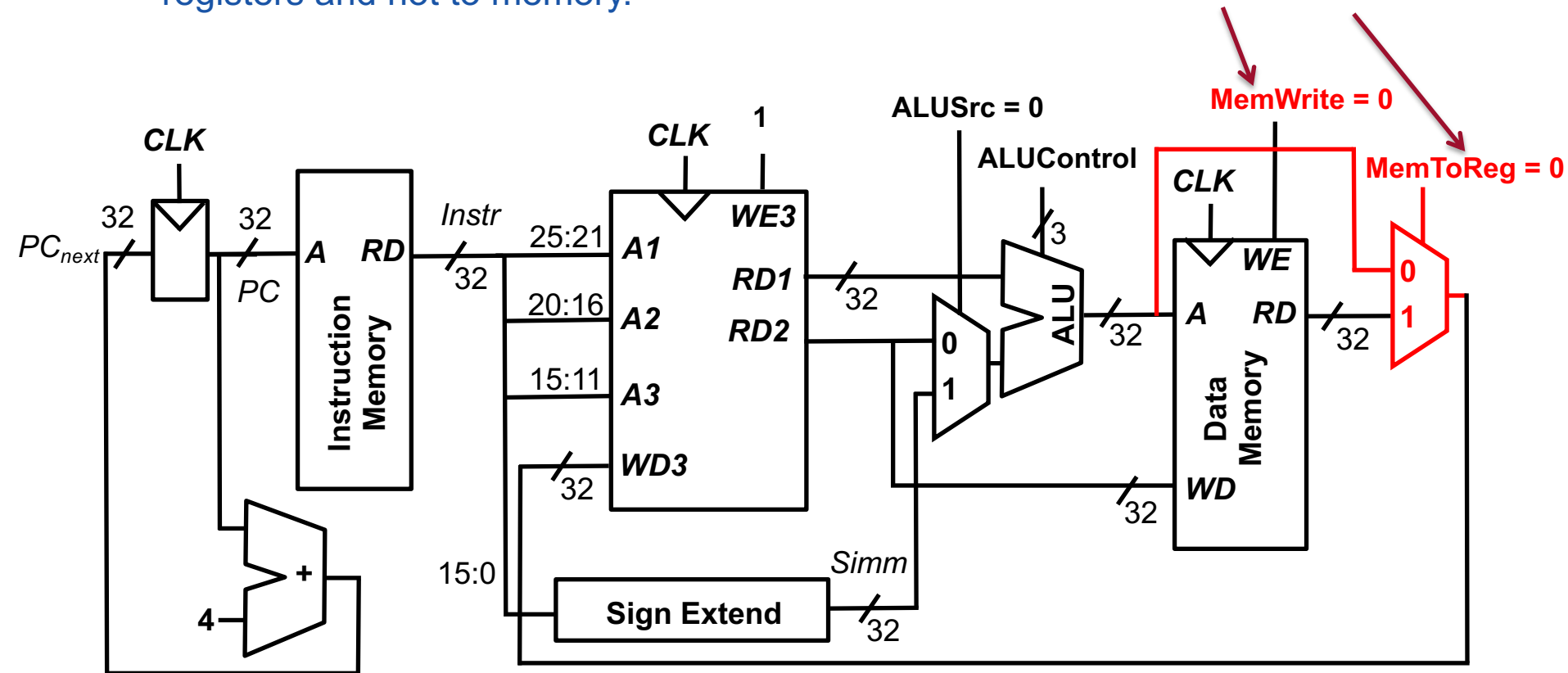
# R-type instructions – Write to Register


R-Type instructions write to registers and not to memory.

Bypass the data memory if an R-Type instruction






# R-type instructions – Machine Encoding

 


 
# beq instruction – Machine Encoding

Recall that the **beq** instruction is a branch instruction, encoded in the I-Type.



Recall how to compute the BTA:


$$\text{BTA} = \text{PC} + 4 + \text{imm} * 4$$

**Example**

**beq**    **\$s0, \$s1, loop**

# beq instruction

Compare if equal

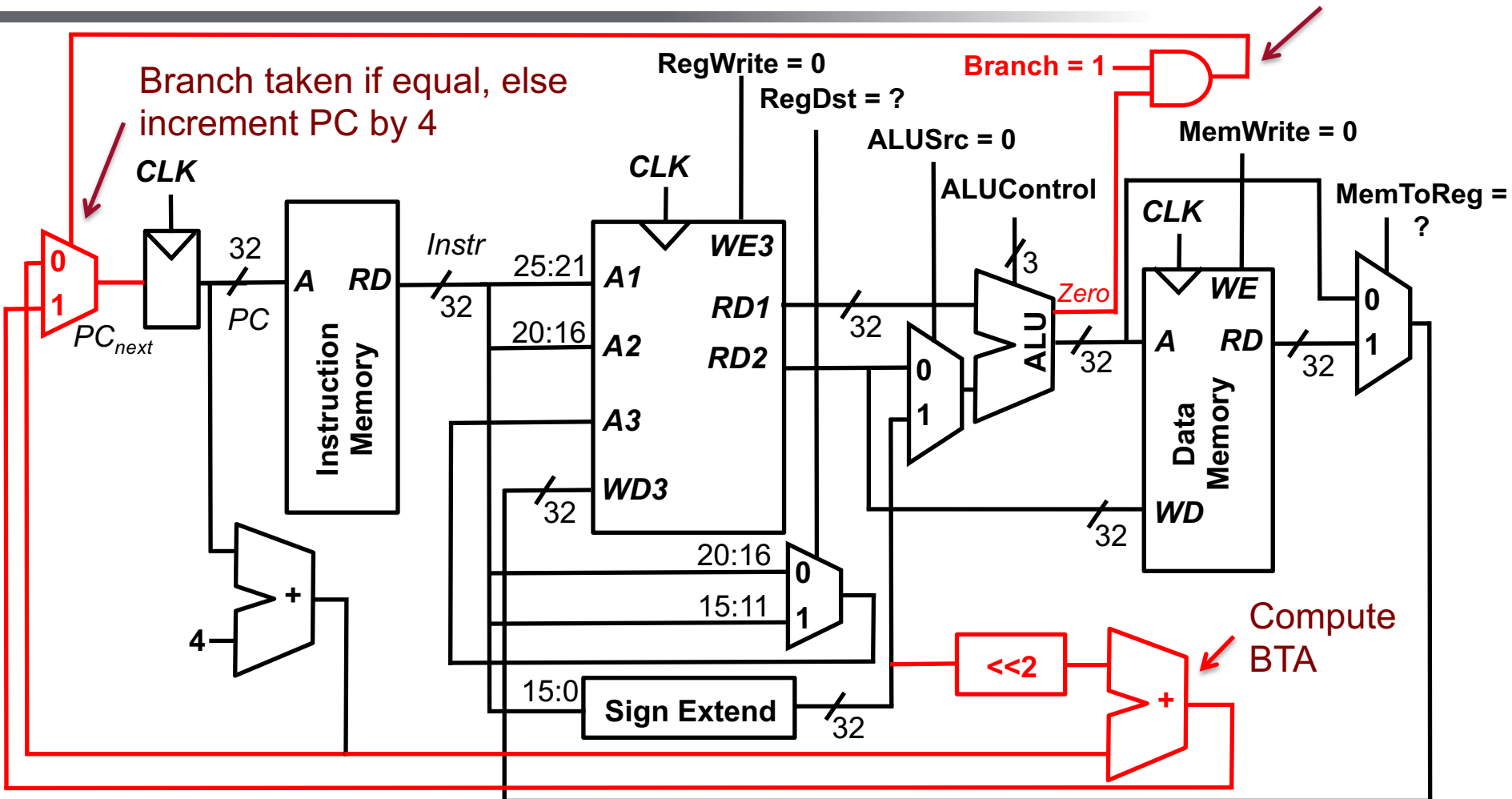

Part I  
Arithmetic  
Logic Unit




Part II  
Data Path in a  
Single-Cycle Processor

Part III  
Control Unit in a  
Single-Cycle Processor
 
# Pseudo-Direct Addressing (Revisited)


The **J** and **JAL** instructions are encoded using the **J-type**. But, the address is not 32 bits, only 26 bits.



A **32-bit Pseudo-Direct Address** is computed as follows:

- Bits 1 to 0 (least significant) are always zero because word alignment of code.
- Bits 27 to 2 is taken directly from the **addr** field of the machine code instruction.
- Bits 31 to 28 are obtained from the four most significant bits from  $PC + 4$ .

# j instruction

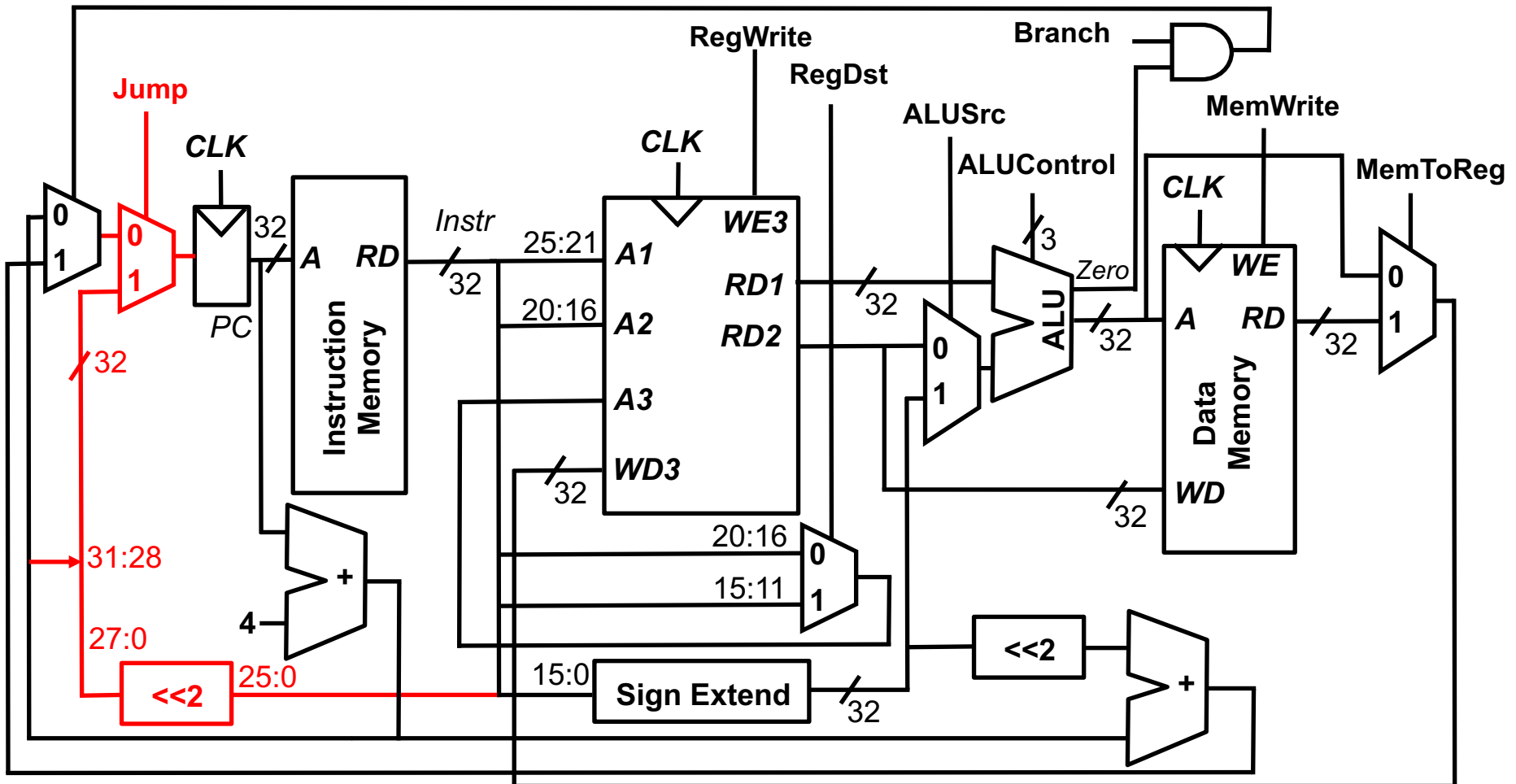

Part I  
Arithmetic  
Logic Unit




Part II  
Data Path in a  
Single-Cycle Processor

Part III  
Control Unit in a  
Single-Cycle Processor

# Data Path for Instructions

`add, sub, and, or, slt, addi, lw, sw, beq, j`

Note: we have indirect support for `addi` (with sign extension), but `ori` would need additional logic.

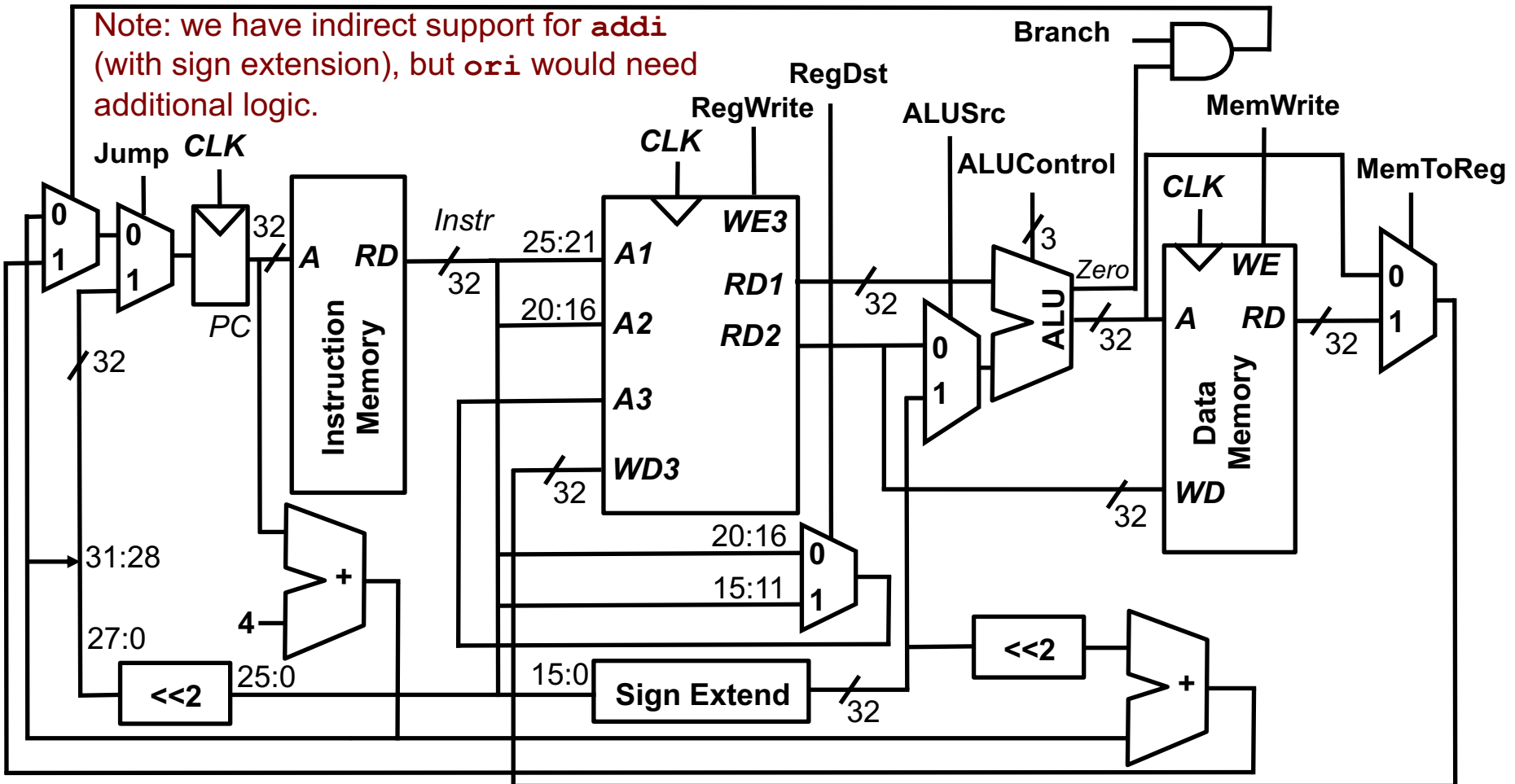

Part I  
Arithmetic  
Logic Unit



Part II  
Data Path in a  
Single-Cycle Processor

Part III  
Control Unit in a  
Single-Cycle Processor

## Part III


# Control Unit in a Single-Cycle Processor



Acknowledgement: The structure and several of the good examples are derived from the book “Digital Design and Computer Architecture” (2013) by D. M. Harris and S. L. Harris.

**Part I**  
Arithmetic  
Logic Unit


**Part II**  
Data Path in a  
Single-Cycle Processor

 **Part III**  
Control Unit in a  
Single-Cycle Processor



# What to Control?

We should set the control signals depending on the instruction.

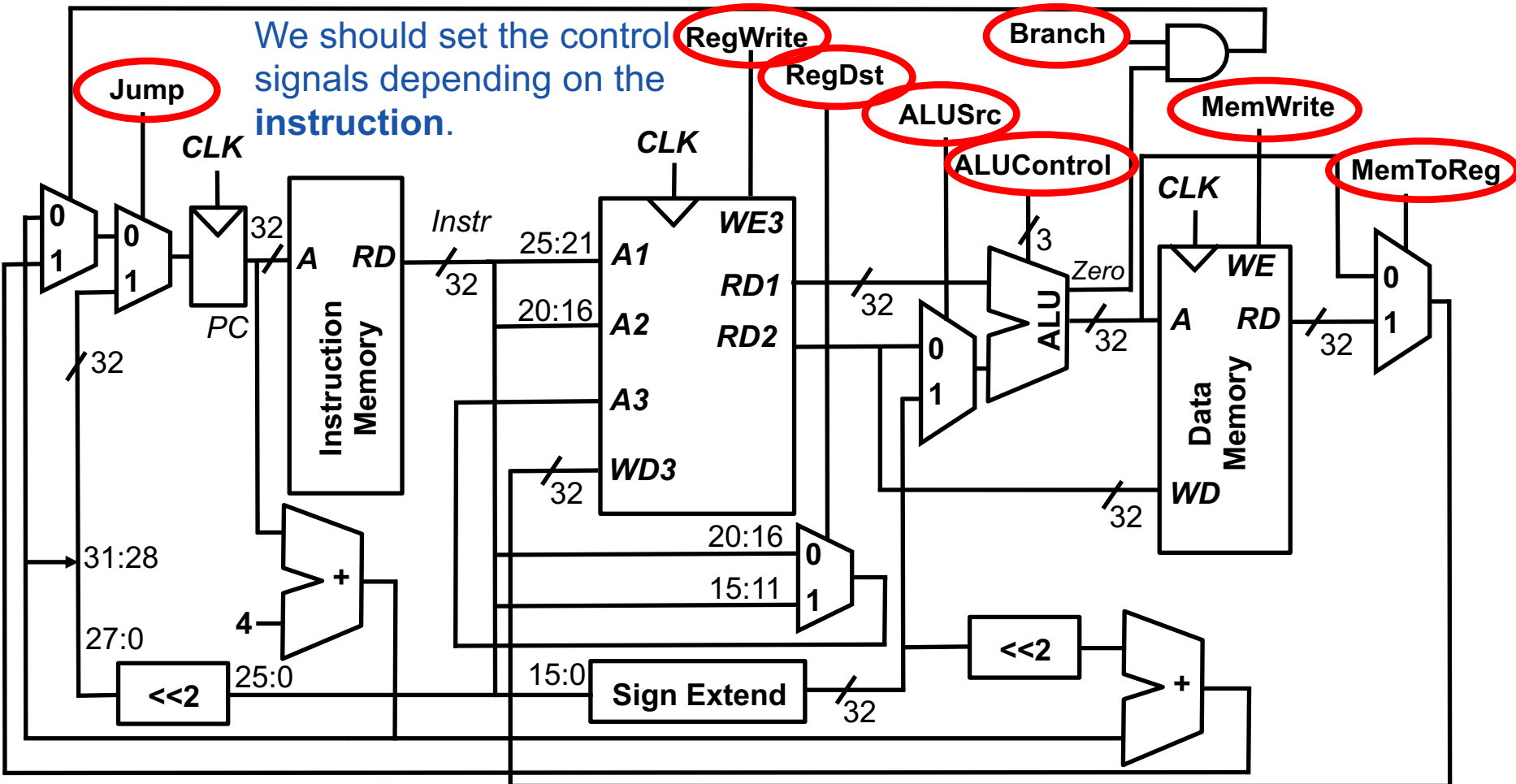

Part I  
Arithmetic  
Logic Unit

Part II  
Data Path in a  
Single-Cycle Processor

Part III  
Control Unit in a  
Single-Cycle Processor


# Control Unit Input: Machine Code

R-Type




For most R-Type instructions, the op field is 0. The control signals depend on the **funct** field.

I-Type

 

For I-Type and J-Type, the control signals depend on the **op** field

J-Type

 

# Control Unit Structure

The 6 bits **op** field from all instruction types

Internal signal ALUOp


ALUOp = 00 means add

ALUOp = 01 means subtract

ALUOp = 10 look at the **funct** field

ALUOp = 11 n/a

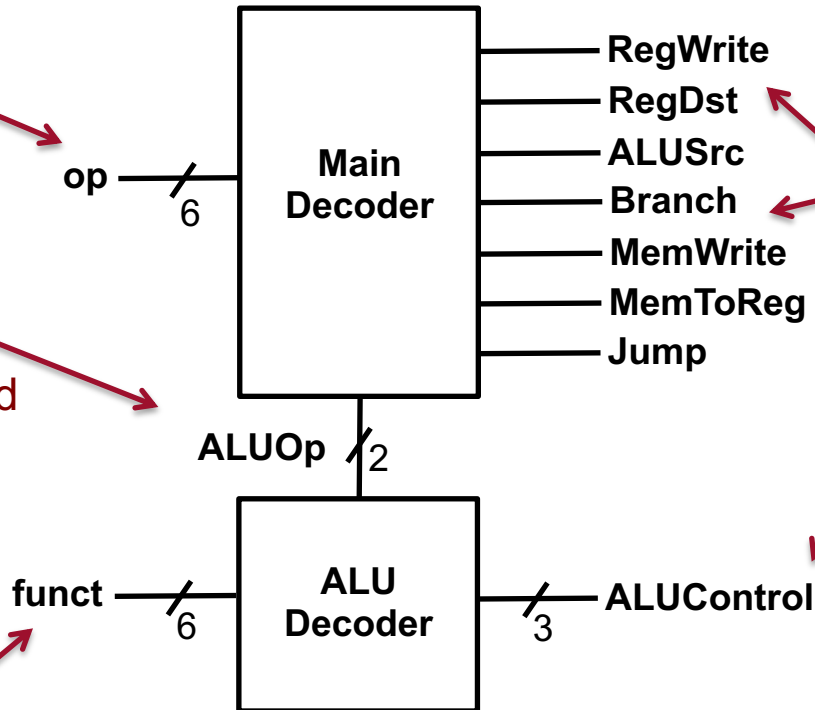
The 6 bits **funct** field from the R-type.  
Ignored if other types.



Control signals to the data path
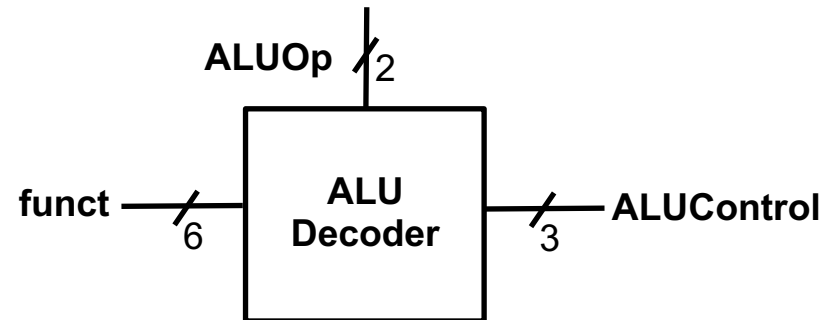
# ALU Decoder

Enough to check one bit (faster decoding)



ALUOp	funct	ALUControl
00	?	010 (add)
?1	?	110 (subtract)
1?	100000 (add)	010 (add)
1?	100010 (sub)	110 (subtract)
1?	100100 (and)	000 (and)
1?	100101 (or)	001 (or)
1?	101010 (slt)	111 (set less than)

# Main Decoder

Instr	op	RegWrite	RegDst	ALUSrc	Branch	MemWrite	MemToReg	Jump	ALUOp
R-Type	000000	1	1	0	0	0	0	0	10
lw	100011	1	0	1	0	0	1	0	00
sw	101011	0	?	1	0	1	?	0	00
beq	000100	0	?	0	1	0	?	0	01
addi	001000	1	0	1	0	0	0	0	00
j	000010	0	?	?	?	0	?	1	??

# Performance Analysis (1/2)

## General View

How should we analyze the performance of a computer?

- By clock frequency?
- By instructions per program?

$$\text{Execution time (in seconds)} = \# \text{ instructions} \times \frac{\text{clock cycles}}{\text{instruction}} \times \frac{\text{seconds}}{\text{clock cycle}}$$

Number of instructions in a program (# = number of)

Determined by programmer or the compiler or both.

Average **cycles per instruction (CPI)**

Determined by the micro-architecture implementation.

Seconds per cycle = **clock period  $T_c$** .

Determined by the critical path in the logic.

### Problem:


- Your program may have many inputs.
- Not only one specific program might be interesting.

### Solution:

Use a **benchmark** (a set of programs).  
Example: SPEC CPU Benchmark

Part I  
Arithmetic  
Logic Unit

Part II  
Data Path in a  
Single-Cycle Processor

 Part III  
Control Unit in a  
Single-Cycle Processor

# Performance Analysis (2/2)

## Single-Cycle Processor

$$\text{Execution time (in seconds)} = \# \text{ instructions} \times \frac{\text{clock cycles}}{\text{instruction}} \times \frac{\text{seconds}}{\text{clock cycle}}$$

Number of instructions in a program (# = number of)

Determined by programmer or the compiler or both.

Average **cycles per instruction (CPI)**

Determined by the micro-architecture implementation.

Each instruction takes one clock cycle. That is,  $\text{CPI} = 1$ .


Seconds per cycle = **clock period  $T_c$** .

Determined by the critical path in the logic.

The main problem with this design is the **long critical path**.

The **lw** instruction has longer path than R-Type instructions. However, because of synchronous logic, the clock period is determined by the slowest instruction.
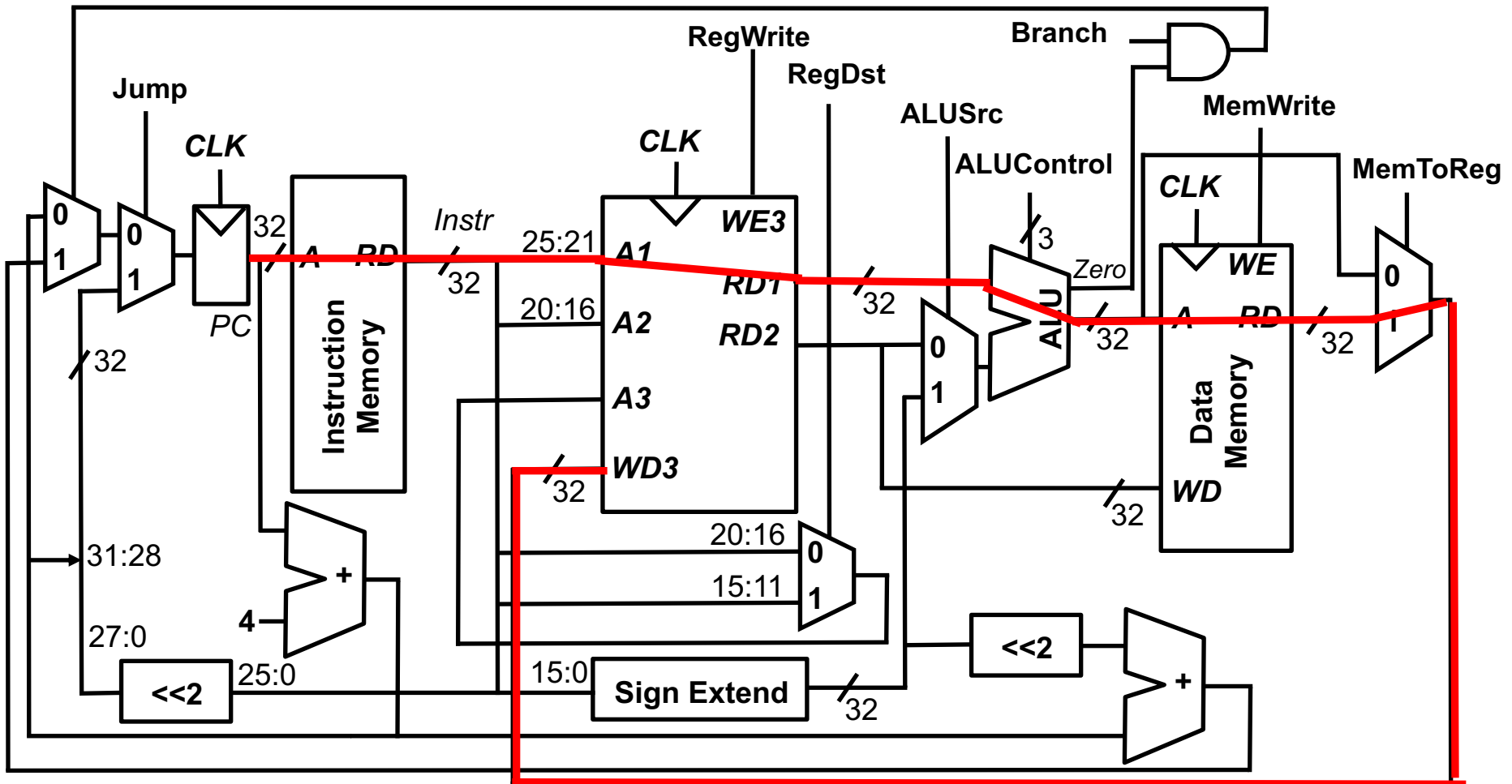
## Critical Path Example: Load Word (lw) Instruction



# Part I Arithmetic Logic Unit

## Part II

### Data Path in a Single-Cycle Processor

## Part III

### Control Unit in a Single-Cycle Processor



**You can soon stretch your legs...**  
**...but wait just a second more**




**Part I**  
Arithmetic  
Logic Unit

**Part II**  
Data Path in a  
Single-Cycle Processor

**Part III**  
Control Unit in a  
Single-Cycle Processor

# Reading Guidelines

 

## Module 4: Processor Design

### Lecture 9: ALU and Single-Cycled Processors

- H&H Chapters 5.2.4, 7.1-7.3.

### Lecture 10: Pipelined processors

- H&H Chapters 7.5, 7.8.1-7.8.2, 7.9

## Reading Guidelines

See the course webpage  
for more information.

**Part I**  
Arithmetic  
Logic Unit

**Part II**  
Data Path in a  
Single-Cycle Processor

**Part III**  
Control Unit in a  
Single-Cycle Processor

# Summary

## Some key take away points:

- The **ALU** performs most of the arithmetic and logic computations in the processor.
- The **data path** consists of sequential logic that performs processing of words in the processor.
- The **control unit** decodes instructions and tells the data path what to do.
- The single-cycle processor has a **long critical path**. We will solve this in the next lecture by introducing a **pipelined processor**.



Thanks for listening!

Part I  
Arithmetic  
Logic Unit

Part II  
Data Path in a  
Single-Cycle Processor

Part III  
Control Unit in a  
Single-Cycle Processor